

24143

**B.Tech. (EE) 4th Semester F-Scheme
Examination, May-2019
DIGITAL ELECTRONICS
Paper-EE-204-F**

Time allowed : 3 hours [Maximum marks : 100]

Note : Attempt five questions in total. All question carry equal marks. Question No. 1 is compulsory. Attempt one question from each unit.

1. (a) Convert :
 - (i) Decimal 145.75 into binary
 - (ii) hexa 4AB4 into octal
- (b) Discuss combinational circuits.
- (c) Difference between latch and flip flop.
- (d) What do you understand by race around condition? <https://www.haryanapapers.com>
- (e) Define hazards and its effects. 5×4=20

Unit-I

2. (a) At the receiver the Hamming code data received is 1011001. Find out the error and also give the correct code. The even parity has been used at transmitter. 10

24143-P-3-Q-9(19)

[P. T. O.]

(2)

24143

- (b) Solve the followings : 2×5=10
 - (i) $\bar{A} + BC + CA - \bar{A}\bar{B}(A - B - C)$
 - (ii) $(A + C + B) + (\bar{B} + C + 1)$
3. (a) Simplify the function using Quine–Mc Clusky method : 15
 $X(A, B, C, D) = m \sum (1, 2, 5, 7, 8, 12, 13)$
- (b) Enumerate Advantages of K Map method. Also give out sequence of actions. 5

Unit-II

4. (a) Explain working of Binary full adder. Also draw the Truth Table. 10
- (b) Discuss working of Comparator with the help of diagram and TT. 10
5. (a) Design 16:1 multiplexer using 4:1 multiplexer. 10
- (b) Design Decimal to Gray encoder. Also give out TT. 10

Unit-III

6. Write short notes on the following : 2×10=20
 - (a) Design of JK Flip flop using SR flip flop
 - (b) Steps involved in state reduction

24143

7. (a) Design module 10 ring counter. Also give out its working and TT. 10
- (b) Enumerate similarities and difference between synchronous and ripple counters. 10

Unit-IV

8. (a) Design PLA using Multiplexer. 10
- (b) Discuss in detail the race free state assignment. 10
9. Write briefly about the following : 7,7,6
- (a) ROM
- (b) ASM design
- (c) PAL