

- (b) Discuss the principle of working of 3 phase bridge inverter with appropriate circuit diagram. Draw phase and line voltage waveform on assumption that each thyristor conducts for  $180^\circ$  and resistive load is star connected. 10

**SECTION – D**

- 8. (a) What is slip power recovery scheme ? Explain working of static Scherbius drive. 10
- (b) Explain volt/hertz method of speed control of 3 phase induction motor. 10
- 9. Discuss why 3-phase to 1-phase Cycloconverter requires positive and negative group phase-controlled converters ? Under what condition group works as inverter and rectifier ? How should the firing angles of two converters be controlled ? 20

Roll No.

**24229**

**B. Tech. 5th Semester (EE) (Common with Special Chance)  
Examination – December, 2019**

**POWER ELECTRONICS**

Paper : EE-317-F

Time : Three Hours ] [ Maximum Marks : 100

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note :** Question No. 1 is *compulsory*. Attempt any *one* question from each Section.

- 1. (a) Mention few drawbacks of self-commutation. 4
- (b) Define Cycloconverter. Give some of its industrial applications. 4
- (c) Define electric drive. How electric drives can be classified ? 4

24229-2000-(P-4)(Q-9)(19)

P. T. O.

- (d) What are the effects of poor power factor ? How this can be improved ? 4
- (e) Define holding current and latching current of SCR. 4

**SECTION – A**

- 2. (a) Describe the working of IGBT and its switching characteristics. 10
- (b) Draw output and transfer characteristics of MOSFET and explain the terms (i) pinch off voltage (ii) threshold voltage and (iii) trans-conductance. 10
- 3. (a) Explain turn-on methods of thyristor. 10
- (b) Define commutation techniques and explain any two of them in detail. 10

**SECTION – B**

- 4. (a) Explain the working principle of single phase ac voltage controller. What is the effect of load inductance on the performance of ac voltage controller ? 10

- (b) A single phase half wave controlled rectifier with  $R = 10 \Omega$  is supplied from 230 V, 50 Hz supply. Assume rms voltage is 50% of maximum possible rms voltage, determine (i) firing angle (ii) average dc output voltage (iii) average and rms current of SCR. 10

- 5. (a) Describe the operation of three phase full converter showing rectification and inversion mode of operation. https://www.mdustudy.com 10
- (b) Explain the working of dual converter with the help of circuit diagram. Also obtain, waveform for voltage generating circulating current. 10

**SECTION – C**

- 6. Explain operation of four quadrant chopper with neat and clean diagram. 20
- 7. (a) Describe McMurray-Bedford half bridge single phase inverter with relevant voltage and current waveform. 10