

B.Tech. 3rd Semester (I.T.) Examination,

December-2016

DIGITAL ELECTRONICS

Paper-EE-204-F

Time allowed : 3 hours] [Maximum marks : 100

Note : The candidate will be required to attempt five questions in all at least one question from each unit.

Question No. 1 is compulsory.

- | | | |
|--------|--|---|
| 1. (a) | What is meant by parity bit ? | 1 |
| (b) | Define duality property. | 1 |
| (c) | State De Morgan's theorem. | 2 |
| (d) | What is encoders and decoders ? | 4 |
| (e) | Define sequential circuits and latches. | 2 |
| (f) | Difference between latches and flip flop. | 2 |
| (g) | What is the difference between PLA and PAL ? | 2 |
| (h) | What is the asynchronous sequential logic ? | 2 |
| (i) | Explain hamming codes with example. | 2 |
| (j) | Define binary codes, cyclic codes, error detecting and error correcting codes. | 2 |

Unit-I

2. (a) Design a simple logic circuit such that the output is 1 when the binary numbers A, B, C, D is greater than 0110. 8
- (b) In a 4-input NAND gate, two inputs are to be used. What are the options available for the unused inputs and which one is the best and why? 7
- (c) What is prime implicants? and state distributive law. 5
3. (a) Perform the following operations on the given binary numbers as specified :
- (i) $110.01 + 1.011$ 1
- (ii) Convert 11101.01 to decimal 1
- (iii) $11100.101 - 101.01$ using 2's complement. 1
- (iv) State whether the following statement is true or false :
 "All decimal fractions have exact binary equivalents" and justify your answer. 2

- (b) Solve the following expression by mapping :

$F = \sum m (0, 2, 3, 6, 7, 8, 9, 10, 13).$

Write the steps involved in solving this Quine-McClusky method. 7

- (c) Perform the operation $(12_{10} - 35_{10})$ using 2's complement method. 2

- (d) Obtain the minimal SOP expression for $Y (A, B, C, D) = \sum m (2, 3, 5, 7, 8, 9, 11, 12, 13, 14, 15) + d (2, 4)$ using k-map. Realize the expression using 2-input NAND gates only. 6

Unit-II

4. (a) Construct a 4-input multiplexer using four 3-input AND gates, an OR gate and three inverters. Show the input, output and select lines and write a table showing the outputs for various select inputs. 8
- (b) Design a combinational circuit that accepts a 3-bit number as input and generates an output binary number equal to square of the input number. 5