

67013

**MCA 1st Semester w.e.f. Dec.
2011 (Old for Re-appears only
with old notes) Examination-
December, 2013**

DIGITAL DESIGN

Paper MCA-103

Time : 3 hours

Max. Marks : 80

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard will be entertained after the examination.

Note : All questions carry equal marks. Attempt **five** questions, selecting at least **one** question from each Unit.

UNIT - I

1. What do you mean by radix of any number system ? Explain any four popular number systems with examples. Also perform the following conversions : 4

- (i) $(101101.10101)_2 = ()_{10}$ 2
- (ii) $(0.10100)_2 = ()_{16}$ 2
- (iii) $(10.675)_{10} = ()_8$ 2
- (iv) +15 and -15 in 1's complement 2
- (v) 00110101 in 2's complement 2
- (vi) +23 in signed magnitude 2

2. Perform the following operations : $4 \times 4 = 16$

(i) (a) Add :

0101 and 1110

(b) 01101010, 00001000 and 11111111

(ii) Multiply :

(a) 1001 and 1101

(b) 0011 and 1111

(iii) Division :

(a) 1110101 by 1001

(b) 11110001 by 1100

(iv) Convert to Octal : $(247)_{10}$ and $(324.6875)_{10}$

UNIT - II

3. (i) What are Semi Conductors ? Explain the working of p-n junction diode in view of forward bias and reverse bias.
- (ii) List down various differences between NMOS and PMOS logic families.
4. (i) Minimize the following logic function, using Boolean Algebra :
- $$F(a,b,c,d) = abcd + abcd + abc + abd + ac + abc + b$$
- (ii) Define the following concepts : SOP, POS, Canonical minterm and maxterm.

UNIT - III

5. Define Flip-Flops. Explain the concept of Edge Triggered and Level Triggered circuits. Describe the structure of 1-bit memory cell (latch). Also outline the working of Master-Slave flip-flop.

6. Differentiate between : (any two)

(i) ROM and RAM

(ii) Encoder and Decoder

(iii) PLA and Arrays

UNIT - IV

7. Why Counters are very popular circuits ?
What are its various applications and types ?
Also design a divide-by-6-counter. What is propagation delay in counters ?

8. (i) How a simple shift register is updated to controlled shift register ?

(ii) Outline the details of RAM architecture.
Which type of RAM is preferred in digital circuits ?